
## SimpleCPU\_v1a

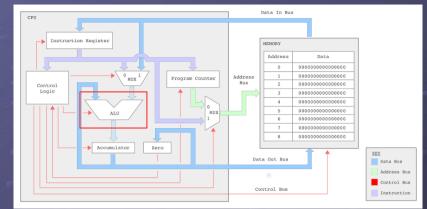

#### Block diagram

Slide 2

ilide 4

ALU : a core requirement of any computer is to process data i.e. the Arithmetic and Logic unit, the ADDER the heart of any CPU. University of York : M Freeman 2021

Slide 1


#### **Binary addition**

University of York : M Freeman 2021

Systems and Devices 1


Lec 3b :


**Combinatorial Logic** 

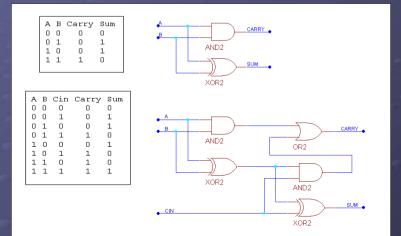

 Half and full adder
 Basic components can be combined into larger circuits University of York : M Freeman 2021


#### Demo : relay logic

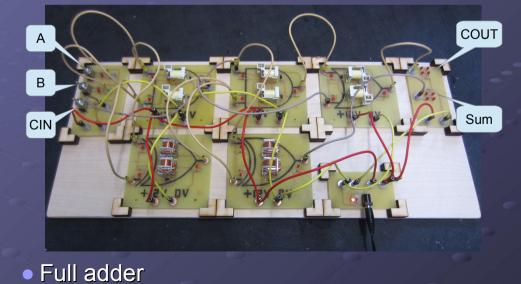

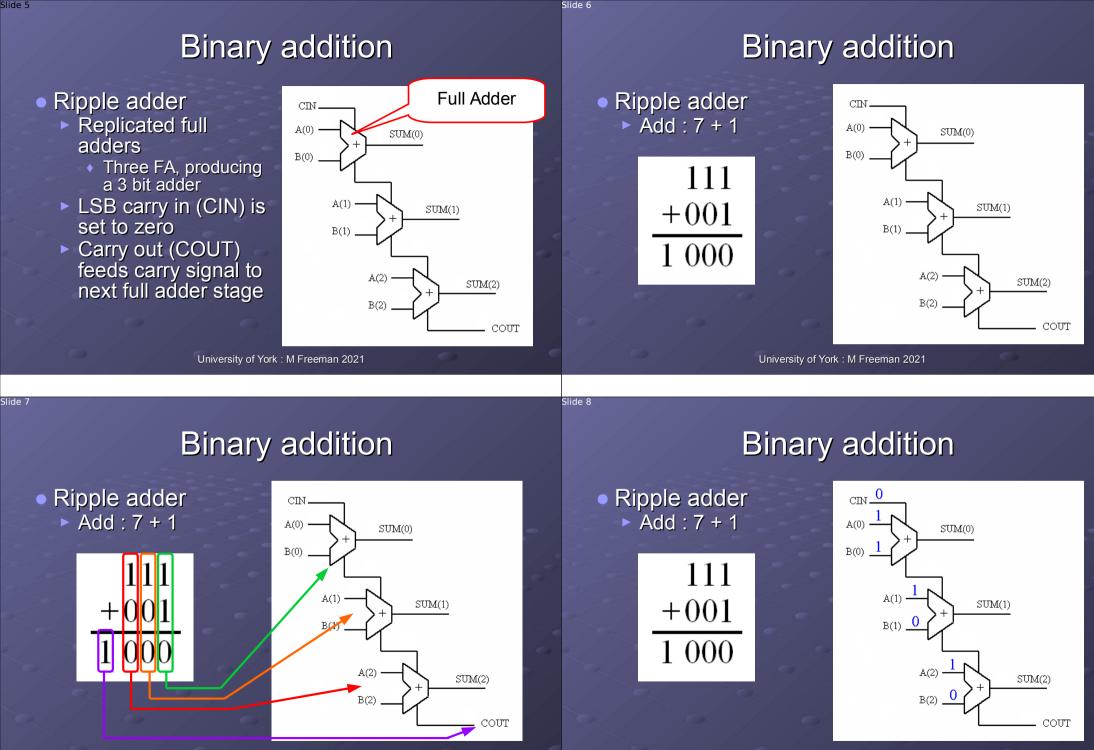


#### **Binary addition**

#### **Binary addition**

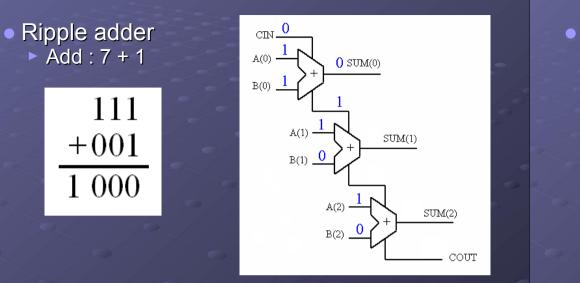

University of York : M Freeman 2021

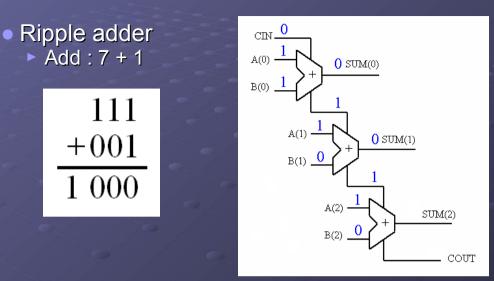



University of York : M Freeman 2021

Slide 11

Slide 9

#### **Binary addition**

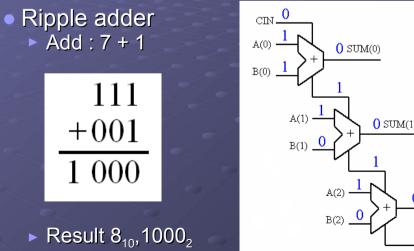

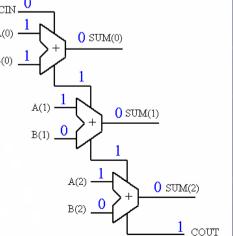

#### **Binary addition**

$$151_{8} + 252_{8} = ?$$

$$+$$

$$100010011$$

$$= 423_{8}$$

#### • Quick Quizzz

Slide 10


Slide 12

- Convert the following values into binary then confirm the result of the binary addition.
- Is the conversion of the binary result to octal correct?

## **Binary addition**
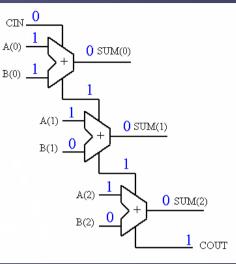
#### • Ripple adder

- MSB Carry Out
  - Can be passed to additional full adder stage to allow larger adders to be constructed.
  - Can be used to indicate that the result has exceeded the maximum bit representation i.e. an overflow has occurred.
- Important, will use these ideas when writing assembly code.




#### **Binary addition**
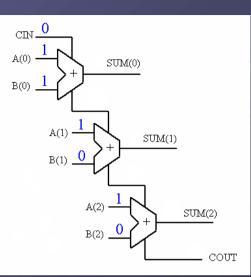
#### Ripple adder

 Remember that hardware is not software i.e. each full adder will operate in parallel.

The result will go through a series of states before it settles down to the final value.




University of York : M Freeman 2021

**Binary addition** 

University of York : M Freeman 2021

Slide 15

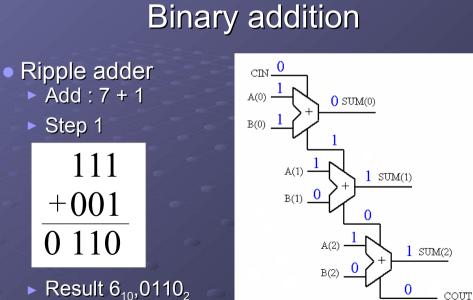


lide 16

Slide 14


Ripple adder
Add : 7 + 1
Step 2

 $\begin{array}{r}
 111 \\
 +001 \\
 \overline{0\ 100}
 \end{array}$ 


▶ Result 4<sub>10</sub>,0100<sub>2</sub>

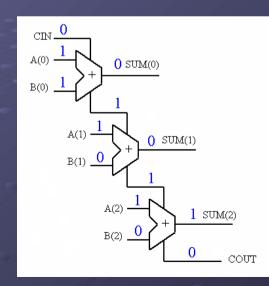

# **Binary addition**

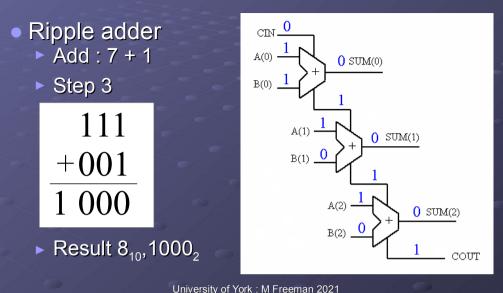

## **Binary addition**

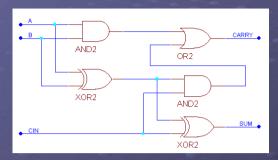


#### Quick Quizz

Slide 18

Slide 20

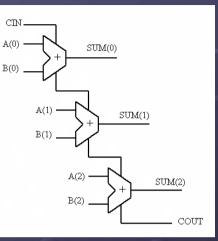If each logic gate takes 10 ns to process a signal, what is the critical path delay of this ripple adder?




University of York : M Freeman 2021

Slide 19

#### Example : adder\_8.zip


| Name       | Value    | 0.0 us   |          | 0.2 us   |          | 0.4 us   |          | 0.6 us   |          | 0.8 us   |
|------------|----------|----------|----------|----------|----------|----------|----------|----------|----------|----------|
| u cin      | 0        |          |          |          |          |          |          |          |          |          |
| ▶ 📑 a[7:0] | 00000000 |          | 00000000 |          | 0000     | 0001     | 00000000 | 1111     | 1110     | 00000000 |
| ▶ 📑 b[7:0] | 0000000  |          | 00000000 |          | 0000     | 0001     | 00000000 | 00000001 | 00000010 | 00000000 |
| sum[7:0]   | 00000000 | 00000000 | 00000001 | 00000000 | 00000010 | 00000011 | 00000000 | 11111111 | 00000000 | 00000000 |
| 1 cout     | 0        |          |          |          |          |          |          |          |          |          |
|            |          |          |          |          |          |          |          |          |          |          |

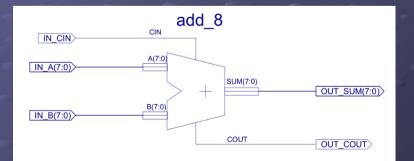

• 8 bit ripple adder

University of York : M Freeman 2021

#### SimpleCPU\_v1a

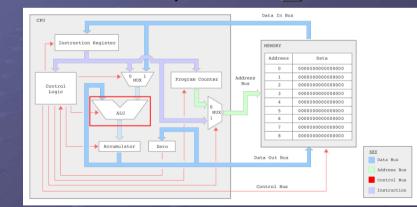

• Block diagram

Q : how do we control the ALU's function e.g. pass through, add, subtract and bitwise AND functions, as defined in the instruction set? How do we implement these functions? University of York : M Freeman 2021

# ALU

| alu           | ALU CTL2 | ALU CTL1 | ALU CTL0 | OP   |
|---------------|----------|----------|----------|------|
|               | 0        | 0        | 0        | ADD  |
| A(7:0) Y(7:0) | 0        | 0        | 1        | SUB  |
|               | 0        | 1        | 0        | AND  |
| B(7:0)        | 0        | 1        | 1        | NU   |
|               | 1        | 0        | 0        | PASS |
| CTL(2:0)      | 1        | 0        | 1        | NU   |
|               | 1        | 1        | 0        | NU   |
|               | 1        | 1        | 1        | NU   |

- ALU interface and control (CTL) signals
  - A(7:0) 8bit input, driven by ACC
  - B(7:0) 8bit input, driven by Data MUX, IR(7:0) or DIN(7:0)
  - CTL(2:0) 3bit input, function select, driven by control logic
  - Y(7:0) 8bit output, result of selected function, Y <= A op B.</p>
- Pass through = multiplexer, addition = ripple adder S
- How do we perform subtraction and bitwise AND?

University of York : M Freeman 2021

# Key skills : working in base 2

| 10010110  | 150 |
|-----------|-----|
| -00101100 | -44 |
|           |     |

Subtract two binary numbers : 150 - 44
 Positive, integer

University of York : M Freeman 2021

Key skills : working in base 2

150

Slide 23

# Key skills : working in base 2

| 10010110  | 150 |
|-----------|-----|
| -00101100 | -44 |
| 0         |     |
|           |     |

- Subtract two binary numbers : 150 44
  - Positive, integer

 $\frac{-00101100}{10}$ 

10010110

Slide 22

ilide 24

Subtract two binary numbers : 150 - 44
 Positive, integer

| 10010110  | 150 |
|-----------|-----|
| -00101100 | -44 |
| 010       |     |


Subtract two binary numbers : 150 - 44
 Positive, integer

University of York : M Freeman 2021

## Key skills : working in base 2

Slide 26

ilide 28

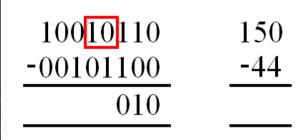

Subtract two binary numbers : 150 - 44
 Positive, integer

University of York : M Freeman 2021

# Key skills : working in base 2


Borrow case

Slide 25


Slide 27


- Look to the left until the first 1 is found, this defining a block i.e. 10...0
- Write a 1 in the result and update block to 01....1
- Continue subtraction
- Alternatively, another way to think of it
  - Borrow '2' from the left column
    - Same process you would perform in base 10, but rather than borrowing 10 you borrow 2

Key skills : working in base 2

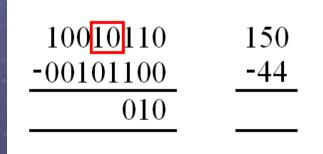

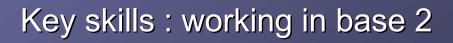Subtract two binary numbers : 150 - 44
 Positive, integer



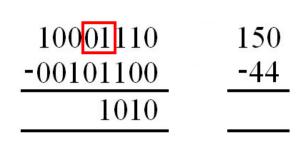

Subtract two binary numbers : 150 - 44
 Positive, integer

University of York : M Freeman 2021

#### Key skills : working in base 2

Slide 30

Slide 32


| 100 <mark>01</mark> 110 | 150 |
|-------------------------|-----|
| -00101100               | -44 |
| 01010                   |     |

Subtract two binary numbers : 150 - 44
 Positive, integer

University of York : M Freeman 2021

Slide 29

#### Key skills : working in base 2

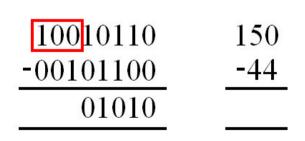


• Subtract two binary numbers : 150 - 44

Positive, integer

Key skills : working in base 2

| 150 |
|-----|
| -44 |
|     |
|     |

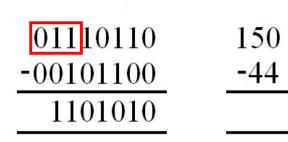Subtract two binary numbers : 150 - 44
 Positive, integer



Subtract two binary numbers : 150 - 44
 Positive, integer

University of York : M Freeman 2021

## Key skills : working in base 2

Slide 34

lide 36

| 01110110  | 150 |
|-----------|-----|
| -00101100 | -44 |
| 01101010  |     |

Subtract two binary numbers : 150 - 44
 Positive, integer

University of York : M Freeman 2021

lide 35

Slide 33

### Key skills : working in base 2

| -44 |
|-----|
| 106 |
|     |

Subtract two binary numbers : 150 - 44

Positive, integer

Method of Complements

| 011 | 010 | 001 | 000           | 111 | 110 | 101 | 100 | • |
|-----|-----|-----|---------------|-----|-----|-----|-----|---|
|     |     |     | $\frac{1}{0}$ |     |     |     |     |   |

- Q : How do we represent negative numbers?
  - Using the complement of a number e.g. 2s complement
  - MSB represents the sign: 0 = +num, 1 = -num
    - Max positive sign bit = 0, MSB –1 to LSB = 1
    - Max negative sign bit = 1, MSB –1 to LSB = 0
- To convert to a Two's complement representation
  - ▶ Invert each bit position (one's complement)  $0 \rightarrow 1$ ,  $1 \rightarrow 0$
  - Add 1 (carry ignored)

#### **2s Complement**

| $1_{10} = 00000001_2$                             | $100_{10} = 01100100_2$  |     | $-100_{10} = 100$                          |
|---|--|-----|--|
| One's Complement : 11111110<br>Add one : 11111111 | One's Complement : 10011011<br>Add one : 10011100  |     | One's Comj<br>Add one :                    |
| $-1_{10} = 11111111_2$                            | $-100_{10} = 10011100_2$   |     | $100_{10} = 011$                           |
| $200_{10} = 11001000_2$                           | <ul> <li>Examples</li> <li>MSB represents the</li> </ul>                                       | - 5 | Eight bit si                               |
| One's Complement : 00110111<br>Add one : 00111000 | number's sign i.e. a<br>signed number.<br>► Maximum value that can<br>be represented is halved |     | $-100_{10} = 1$<br>$100_{10} = 0$          |
| $-200_{10} = 00111000_2$ ???                      | compared to an unsigned<br>representation  |     | <ul> <li>Note, wh<br/>forgot to</li> </ul> |
| University of Yor                                 | k : M Freeman 2021   |     |  |

Slide 38

Slide 40


# 2s Complement

|   | $-100_{10} = 10011100_2$<br>One's Complement : 01100011<br>Add one : 01100100<br>$100_{10} = 01100100_2$ | <ul> <li>To determine the absolute value of a negative binary number</li> <li>Take the Two's complement again</li> </ul> |  |  |  |  |
|---|--|--|--|--|--|--|
| $\geq$  | Eight bit signed number  | Sixteen bit signed number  |  |  |  |  |
|   | $\begin{array}{l} \textbf{-100}_{10} = 10011100_2 \\ 100_{10} = 01100100_2 \end{array}$                  | $\begin{array}{rcl} -100_{10} &=& 1111111110011100_2 \\ 100_{10} &=& 0000000001100100_2 \end{array}$                     |  |  |  |  |
| <ul> <li>Note, when changing the size of a number don't forgot to sign extend.</li> </ul> |  |  |  |  |  |  |

niversity of York : M Freeman 2021

Slide 39

#### **Binary subtraction**

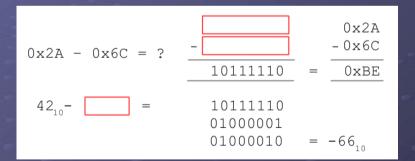


#### • Quick Quizzz

- Convert the following values into binary then confirm the result of the binary subtraction.
- Is the conversion of the binary result to hexadecimal correct?

### **Binary subtraction**

University of York : M Freeman 2021

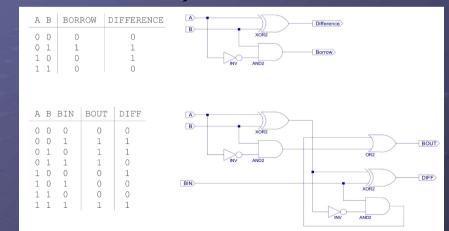

• We could implement the subtraction operation using half and full subtractors, but ...

| 010010110  | 150 |
|------------|-----|
| -000101100 | -44 |
|            |     |

 Using the Two's complement representation simplifies binary subtraction i.e. can be performed using addition

• A - B = A + (-B)

University of York : M Freeman 2021

# Key skills : working in base 2

| 010010110  | 150 |
|------------|-----|
| +111010100 | -44 |
|            |     |

 Using the Two's complement representation simplifies binary subtraction i.e. can be performed using addition A - B = A + (-B)

University of York : M Freeman 2021

Slide 43

### Key skills : working in base 2

| 010010110  | 150 |
|------------|-----|
| +111010100 | -44 |
| 0          |     |
|            |     |

• Using the Two's complement representation simplifies binary subtraction i.e. can be performed using addition ► A - B = A + (-B)

Slide 42

ilide 44

► A - B = A + (-B)

Key skills : working in base 2

| 010010110  | 150 |
|------------|-----|
| +111010100 | -44 |
| 10         |     |
|            |     |

 Using the Two's complement representation simplifies binary subtraction i.e. can be performed using addition

| 010010110  | 150 |
|------------|-----|
| +111010100 | -44 |
| 010        |     |
| 1          |     |

 Using the Two's complement representation simplifies binary subtraction i.e. can be performed using addition
 A - B = A + (-B)

University of York : M Freeman 2021

# Key skills : working in base 2

Slide 46

Slide 48

| 010010110                 | 150 |
|---------------------------|-----|
| $\frac{+111010100}{1010}$ | -44 |
| 1                         |     |

 Using the Two's complement representation simplifies binary subtraction i.e. can be performed using addition
 A - B = A + (-B)

University of York : M Freeman 2021

Slide 47

Slide 45

#### Key skills : working in base 2

| 010010110  | 150 |
|------------|-----|
| +111010100 | -44 |
| 01010      |     |
| 1 1        |     |

 Using the Two's complement representation simplifies binary subtraction i.e. can be performed using addition
 A - B = A + (-B)

University of York : M Freeman 2021

# Key skills : working in base 2

| 010010110  | 150 |
|------------|-----|
| +111010100 | -44 |
| 101010     |     |
| 1 1        |     |

 Using the Two's complement representation simplifies binary subtraction i.e. can be performed using addition
 A - B = A + (-B)

| 010010110  | 150 |
|------------|-----|
| +111010100 | -44 |
| 1101010    |     |
| 1 1        |     |

 Using the Two's complement representation simplifies binary subtraction i.e. can be performed using addition
 A - B = A + (-B)

University of York : M Freeman 2021

#### Key skills : working in base 2

Slide 50

Slide 52

| $010010110 \\ +111010100$ | 150<br>-44 |
|---------------------------|------------|
| 01101010                  |            |
| 1 1 1                     |            |

 Using the Two's complement representation simplifies binary subtraction i.e. can be performed using addition
 A - B = A + (-B)

University of York : M Freeman 2021

Slide 51

Slide 49

# Key skills : working in base 2

| 010010110  | 150 |
|------------|-----|
| +111010100 | -44 |
| 001101010  | 106 |
| 11 1 1     |     |

 Using the Two's complement representation simplifies binary subtraction i.e. can be performed using addition
 A - B = A + (-B) Key skills : working in base 2


| 010010110  | 150 |
|------------|-----|
| +111010100 | -44 |
| 001101010  | 106 |
| 11 1 1     |     |

 Using the Two's complement representation simplifies binary subtraction i.e. can be performed using addition
 A - B = A + (-B)

## Addition of negative numbers

- When using Two's complement representation the carry bit can no longer be used to indicate an overflow.
  - Oveflow number (result) can not be represented by the maximum number of bits within a memory location or register i.e. need more bits, can not be stored.
- Overflow is determined by these rules
  - If operand sign bits are equal then result sign bit must equal operand sign bit
    - E.g. (A + B) or (-A + -B) magnitude always bigger
  - If operand sign bit are not equal then overflow can not occur
    - E.g. (A B) or (-A + B) magnitude always smaller
       University of York : M Freeman 2021

#### Addition of negative numbers

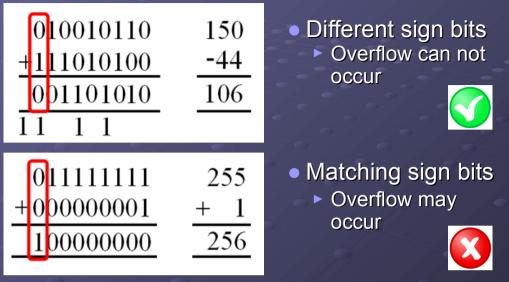


University of York : M Freeman 2021

Slide 55


Slide 53

### Adder / Subtractor unit

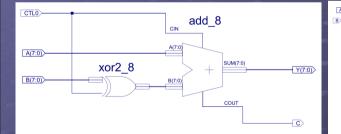

- How do we perform 2's complement in hardware?
  - ADD\_SUB\_8
    - Ripple adder
    - XOR array

### SimpleCPU\_v1a

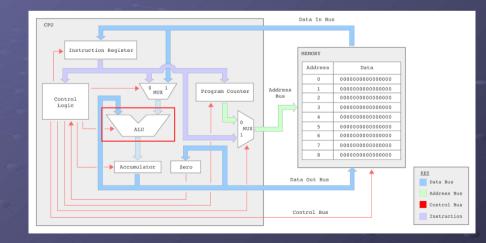


Block diagram

Slide 54

ilide 56

Q : what else is inside the ALU? University of York : M Freeman 2021


# ALU

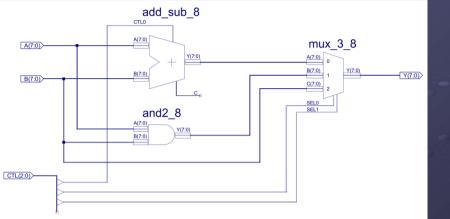

• A : not a lot, a simple ALU for a simple instruction set


Q : what will happen to the CPD if we have more, "complex" (multiply, divide, square root) instructions? University of York : M Freeman 2021

#### ALU

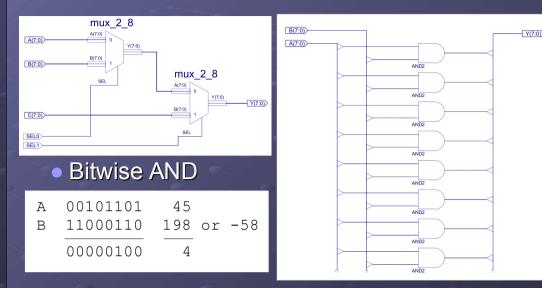

University of York : M Freeman 2021

Summary

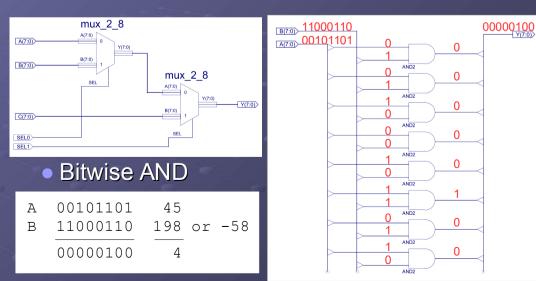

#### ALU

• Key concepts :

Slide 58

Slide 60

- Binary arithmetic
  - Half subtractor, Full subtractor and Ripple subtractor
  - Representing negative numbers 2's complement
  - Subtraction using addition of a negative number
    - Detecting overflows when using signed data
- Data processing : Arithmetic & Logic Unit (ALU)
  - Pass, Add, Subtract and Bitwise AND
  - More complex functions can be construction in software using these basic binary operators e.g. multiply, divide etc.